



---

# AUDIO AMPLIFIER

---

Supervisor by: Dr. Eman Sawires



references From: [1] Floyd, "Electronic Devices", 9th-edition.

## Team Members:



- 1- Mahmoud Abd ElMoneam Ramadan Mohamed
- 2- Mahmoud Khaled Ramadan Ibrahim
- 3- Mosab Mohamed Sayed
- 4- Mostafa Salah Mahdy
- 5- Abd El Rahman Yahia Sayed


## Content →

- 1- Proteus for DC Analysis and AC Analysis page (3-4)
- 2- DC Analysis page (5-7)
- 3- AC Analysis From (8-9)
- 4- Frequency Analysis FL, FH (10-11)
- 5- Power Amplifier Analysis (12)

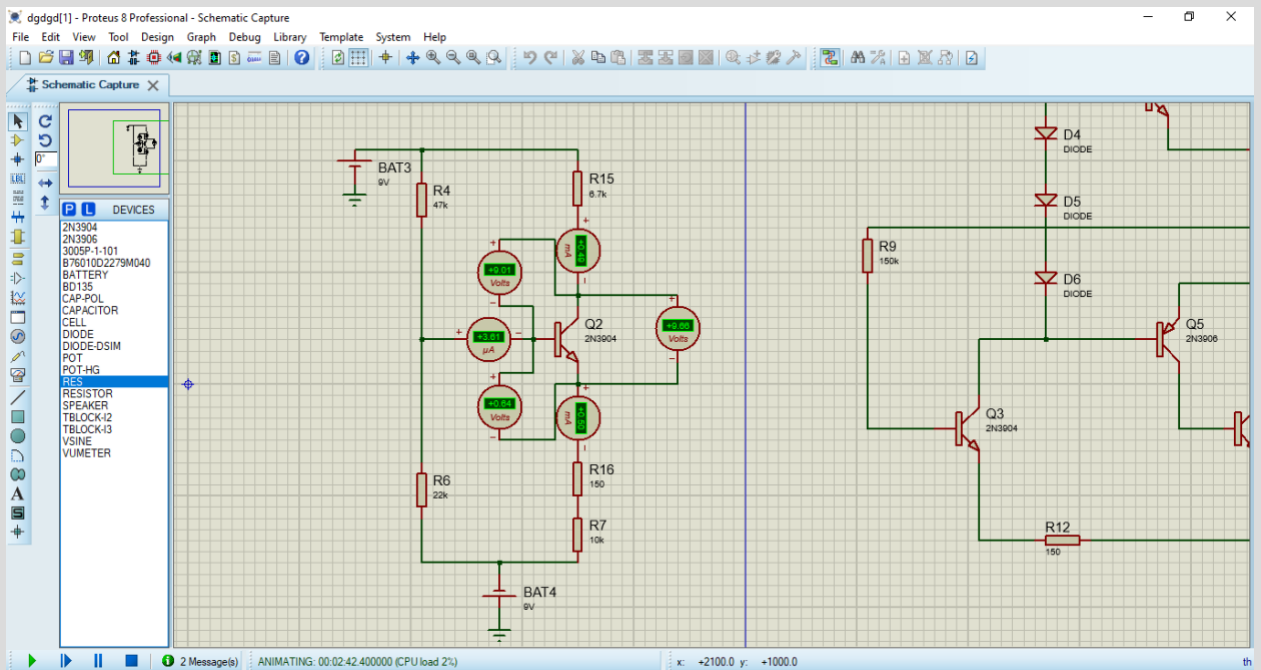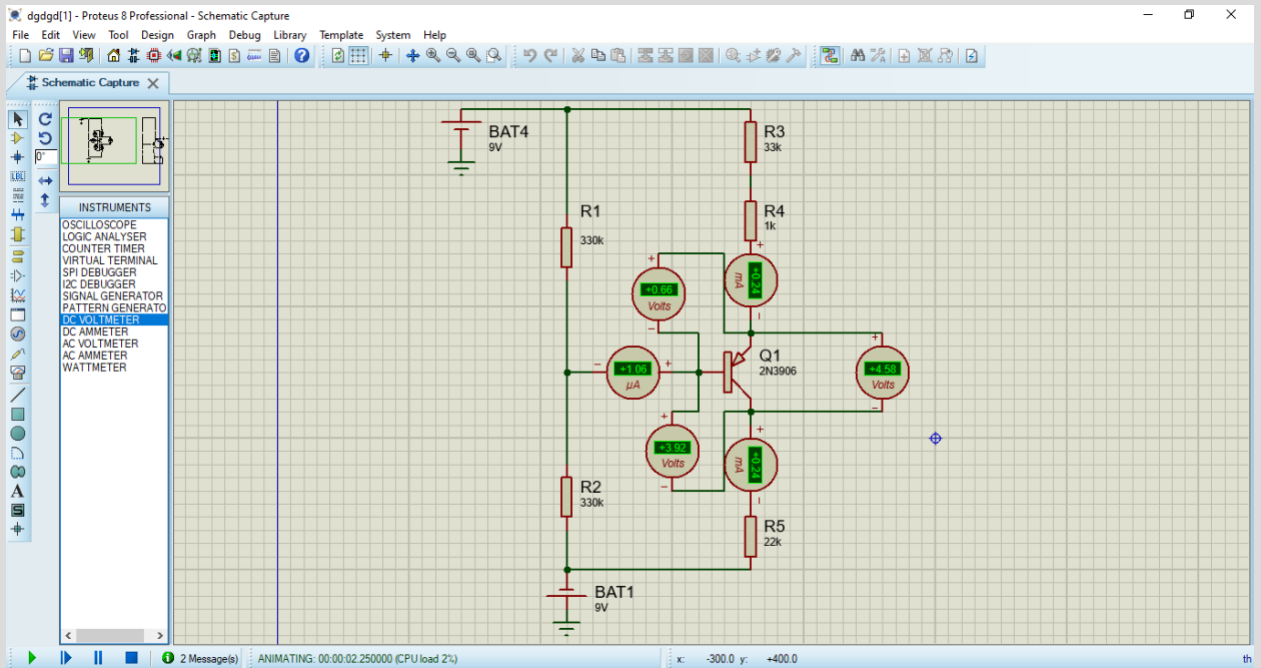
## Steps →

- 1- We do DC Analysis to make Q point in mid-point.
- 2- We do DC Analysis on proteus.
- 3- We calculate Gain and Frequency response and AC Analysis
- 4- And we apply them in proteus.
- 5- We calculate DC analysis for power amplifier.
- 6- We apply the circuit on testboard and it works.
- 7- Finally, we apply it on PCP.



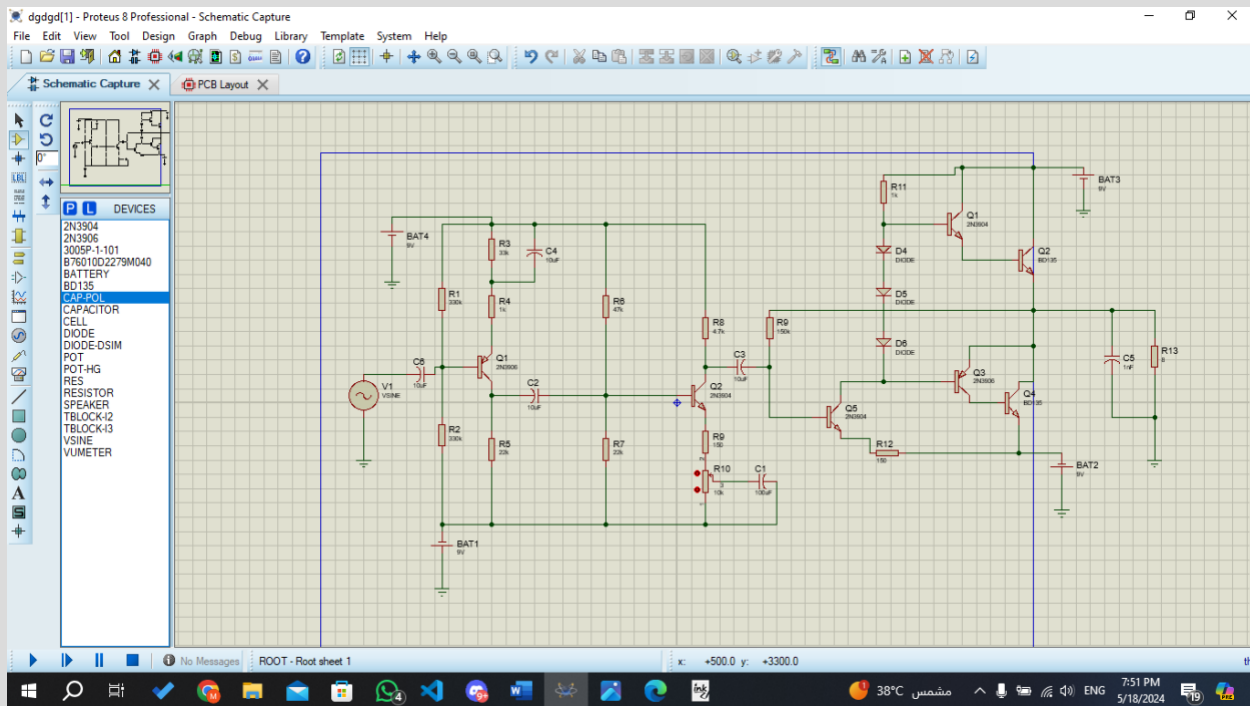

## DC Analysis

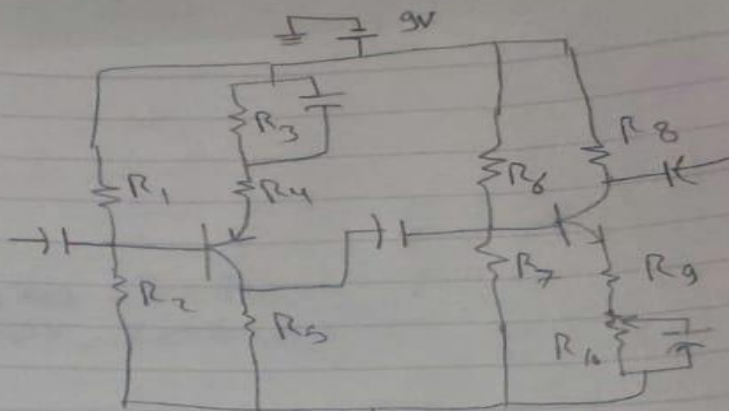

First circuit DC

$$V_{th1} = \frac{9 \times R_1}{R_1 + R_2} = \frac{9 \times 330}{330 + 330} = 4.5 \text{ V}$$

$$V_{th2} = \frac{-9 \times R_2}{R_1 + R_2} = -4.5 \text{ V}$$

$$V_{th} = V_{th1} + V_{th2} = 0$$

$$R_{th} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = 165 \text{ k}\Omega$$

IP Loop

$$9 - I_E (R_3 + R_4) - V_{BE} - I_B R_{th} = 0 \quad (1)$$

$$I_E = (\beta + 1) I_B = 201 I_B \quad (2)$$

$$\therefore 9 - 201 I_B (34 \times 10^3) - 0.7 - I_B \times 165 \times 10^3$$

$$\therefore 8.3 = 6999 \times 10^3 I_B$$

$$\therefore I_B = 1.187 \text{ }\mu\text{A}$$

$$I_C = \beta I_B = 0.237 \text{ mA}$$

$$I_E = (\beta + 1) I_B = 0.2386 \text{ mA}$$

$$g_{m1} = \frac{I_C}{V_T} = \frac{0.237 \times 10^{-3}}{25 \times 10^{-3}} = 9.48 \text{ mA/V}$$

$$V_{\pi 1} = \frac{V_T}{I_B} = \frac{25 \times 10^{-3}}{1.187 \times 10^{-6}} = 21.06 \text{ k}\Omega$$

OP loop

$$9 + 9 - I_E (R_3 + R_4) + V_{CE} - I_C R_5 = 0$$


$$\therefore -V_{CE} = 18 - I_E (34 \times 10^3) - I_C (22 \times 10^3)$$

$$-V_{CE} = 4.673$$

$$\therefore V_{EC} = 4.673$$

$$\therefore V_{EB} = 0.7$$
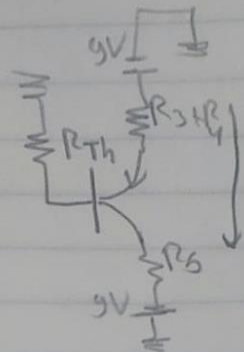
$$\therefore V_{CB} = V_{EB} - V_{EC} = 0.7 - 4.67 = -3.97V$$





second stage DC:

$$R_{th} = R_6 \parallel R_7 = \frac{R_6 * R_7}{R_6 + R_7} = 14.98K\Omega$$

$$V_{th1} = 9V \times \frac{R_7}{R_7 + R_8} = 9V \times \frac{22}{22 + 47} = 2.86V$$

$$V_{th2} = -9V \times \frac{R_6}{R_6 + R_7} = -9V \times \frac{47}{22 + 47} = -6.14V$$

$$V_{th(t)} = V_{th1} + V_{th2} = -3.2704V$$

INPUT Loop:

$$V_{th(t)} + 9 - I_B(R_{th}) - V_{BE} - I_E(R_9 + R_{L0}) = 0$$

$$-3.2704 + 9 - I_B(14.98K) - 0.7 - (2\beta + 1)I_B(19.5K) = 0$$

$$I_B = 2.447 \mu A$$


$$I_C = \beta I_B = 4.89 \times 10^{-4} A$$

$$I_E = (1 + \beta) I_B = 4.91 \times 10^{-4} A$$

$$V_{R2} = \frac{I_C}{V_L} = \frac{4.89 \times 10^{-4}}{0.025} = 0.01956 V = 19.56 mV$$

$$r_{\pi 2} = \frac{V_t}{I_B} = \frac{0.025}{2.447 \times 10^{-6}} = 10.216K\Omega$$

## AC Analysis

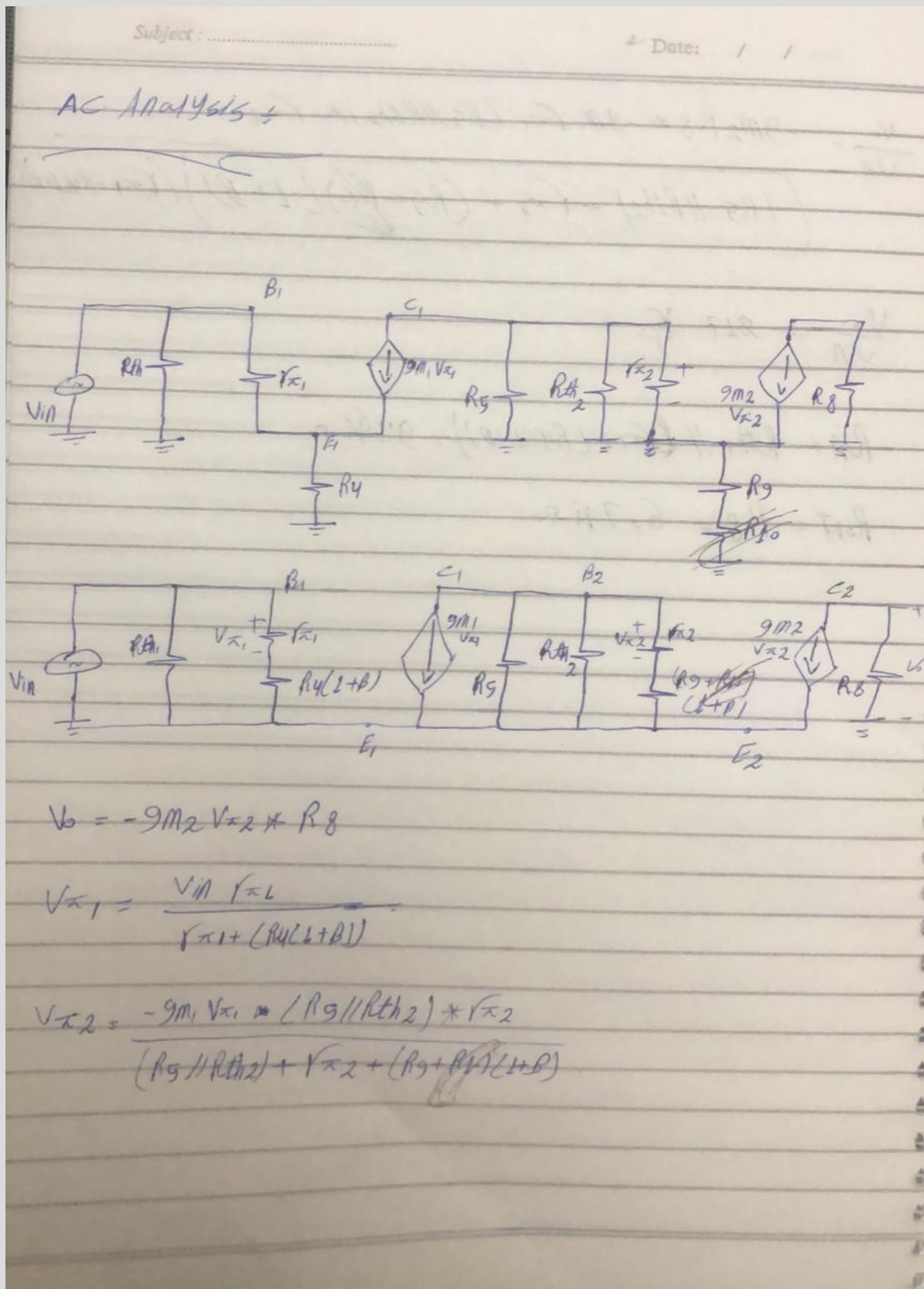



Subject: .....

Date: / /

$$\frac{V_o}{V_{in}} = \frac{-g_{m2} R_8 + -g_{m1} r_{\pi 1} (R_5 \parallel R_{th2}) + r_{\pi 2}}{\left[ (R_5 \parallel R_{th2}) + r_{\pi 2} + (R_9 + R_{th1}) (1 + \beta) \right] (r_{\pi 1} + R_4 (1 + \beta))}$$

$$\frac{V_o}{V_{in}} = 217 \frac{V}{V}$$

$$R_{th1} = R_{th1} \parallel (r_{\pi 1} + (R_4 (1 + \beta))) = 94.61 \Omega$$

$$R_{out} = R_8 = 6.7 k\Omega$$



Subject: .....

Date: / /

FH in first stage:

$C_{\pi}$  in data sheet is: 12 pF


$C_M$  in data sheet is: 4 pF

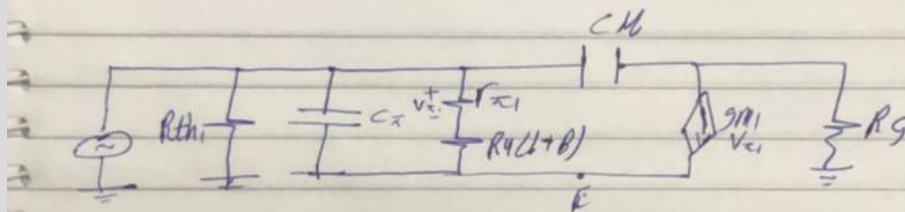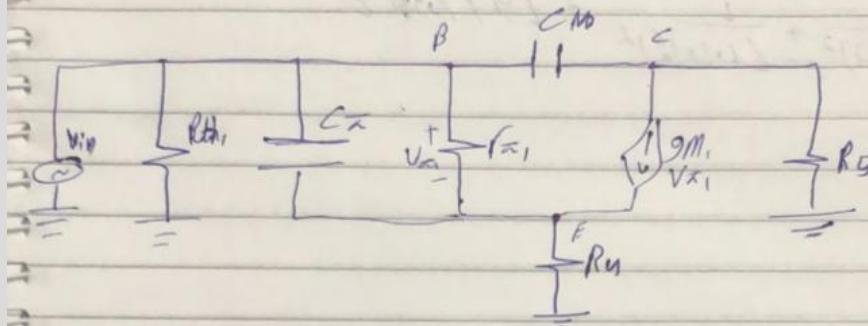

$$A_{vF=0} \sim A = -g_{m1} V_{x1} R_S = -g_{m1} R_S$$

$$C_i = C_{\pi} + C_1 = 12 + 4(1 + g_{m1} R_S) = 89.02 \text{ pF}$$
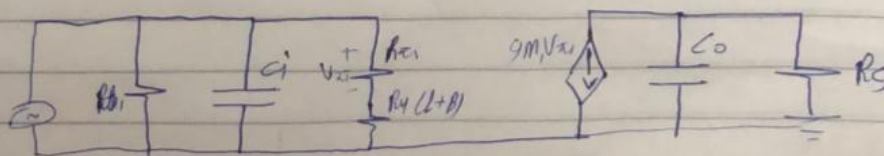
$$C_o = C_{\pi} = C_M \left( 1 - \frac{1}{-g_{m1} R_S} \right) = 4.019 \text{ pF}$$



$$R_{o1} = (R_{th1} \parallel (r_{\pi1} + R_E(1 + \beta))) = 94.66 \text{ k}\Omega$$

$$F_{H1} = \frac{1}{2\pi (94.66 \times 10^3)(89.02 \times 10^{-12})} = 1977.57 \text{ Hz}$$

$$F_{LTotal} = \sqrt{(9.18)^2 + (8.75)^2} = 12.686 \text{ Hz}$$

Using Miller

$$C_1 = C_M (1 - A)$$

$$C_2 = C_M (1 - \frac{1}{A})$$

$$A = \frac{V_o}{V_{\pi 2}}$$

$$V_o = -g_{m2} V_{\pi 2} R_8$$

$$A = -g_{m2} R_8 = -9.2 \text{ V/V}$$

$$C_1 = C_M (1 + 9.2) = 0.372 \text{ nF}$$

$$C_2 = C_M (1 + \frac{1}{9.2}) = 4.04 \text{ pF}$$

$C_M$  in data sheet is 4 pF

$C_{\pi}$  in data sheet is 8 pF

$$\therefore C_{in} = C_1 + C_{\pi} = 12.04 \text{ pF} \quad 380 \text{ pF}$$

$$C_{o1} = C_2 = 4.04 \text{ pF}$$

$$F_{P1} = \frac{1}{2\pi C_{in} R_{eq}}$$

$$R_{eq} = R_{th2} \parallel (V_{\pi 2} + R_9(1+\beta))$$




$$= 10.9 \text{ k}\Omega$$

$$F_{P1} = 38.33 \text{ kHz}$$

$$F_{P2} = \frac{1}{2\pi C_o R_{eq}}$$

$$R_{eq} = R_8 = 4.7 \text{ k}\Omega$$

$$F_{P2} = 8.38 \text{ MHz}$$

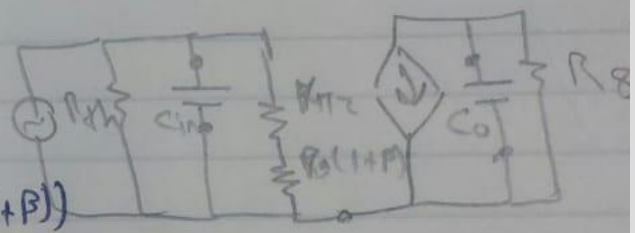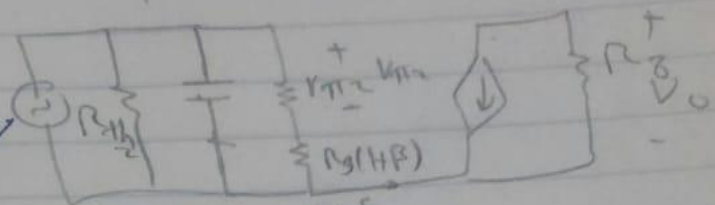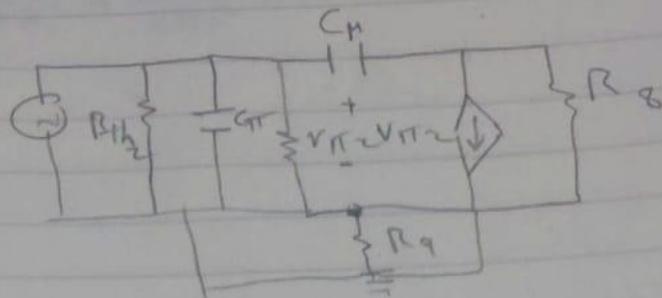

$$F_{H2} = 1 / \sqrt{\frac{1}{F_{P1}^2} + \frac{1}{F_{P2}^2}} = 38.33 \text{ KHz}$$

$$\therefore F_{H_{total}} = \frac{1}{\sqrt{\frac{1}{F_{H1}^2} + \frac{1}{F_{H2}^2}}} = 1974.9 \text{ Hz}$$

$$F_{H2} = 1 / \sqrt{F_{P1}^2 + F_{P2}^2} = 38.33 \text{ KHz}$$

$$\therefore F_{H_{\text{total}}} = \frac{1}{\sqrt{\frac{1}{F_{H1}^2} + \frac{1}{F_{H2}^2}}} = 1974.9 \text{ Hz}$$

$$V_{B3} = 3V - 0.7 = -2.1V$$

$$V_{E3} = V_{EB} + V_B$$

$$V_{E3} = 0.7 - 2.1 = -1.4V$$

$$V_{E1} = V_{B1} - V_{BE1}$$

$$= 2.1 - 0.7 = 1.4V$$

$$V_0 = V_E \text{ of } Q_1 \text{ and } Q_3 = 1.4V$$


Current of  $R_2$

$$I_{R2} = \frac{9 - 1.4}{1k} = 7.6 \text{ mA} \therefore I_{C1} = 7.6 \text{ mA}$$

$$I_{R3} = \frac{1.4 + 9}{220} = 47.2 \text{ mA} \therefore I_{C3} = 47.2 \text{ mA}$$

$$\text{Assuming } \beta = 100 \therefore I_{B2} = \frac{I_{C2}}{\beta} = 76 \mu A$$
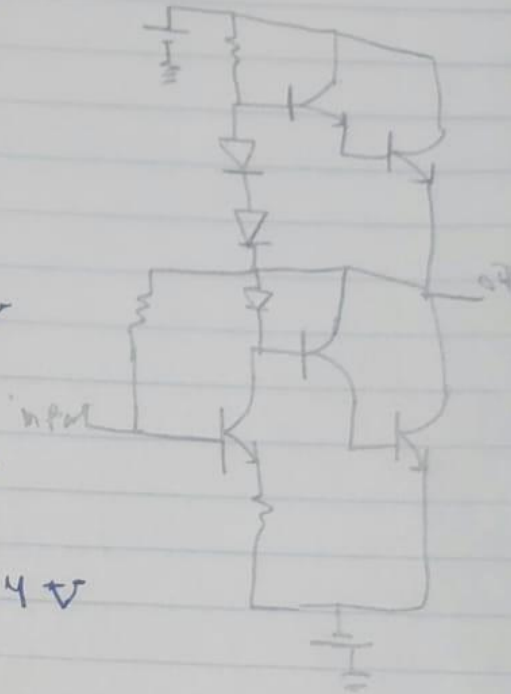
$$I_{B4} = \frac{I_{C4}}{\beta} = 472 \mu A$$





$$I_{C1} = 7.6 \text{ mA} , I_{B1} = 38 \text{ }\mu\text{A}$$

$$I_{E1} = 7.64 \text{ mA}$$

$$I_{B2} = I_{E1} = 7.64 \text{ mA} , I_{C2} = 1.52 \text{ A}$$

$$I_{E2} = 1.53 \text{ A}$$

$$I_{C3} = 47.2 \text{ mA} , I_{B3} = 236 \text{ }\mu\text{A}$$

$$I_{E3} = 47.43 \text{ mA}$$

$$I_{B4} = I_{C3} = 47.2 \text{ mA} , I_{C4} = 9.44 \text{ A}$$

$$I_{E4} = 9.5 \text{ A}$$

$$I_{C5} = I_{B4} = 236 \text{ }\mu\text{A} , I_{B5} = 1.18 \text{ mA}$$

$$I_{E5} = 1.2 \text{ mA}$$

Comparison between DC, AC in proteus and Analysis :

DC, AC values	Proteus	Analysis
$I_{b1}$	1.06 micro	1.16 micro
$I_{e1}$	.245 m	.237 m
$I_{c1}$	.243 m	.238 m
$I_{b2}$	3.61 micro	2.44 micro
$I_{e2}$	.50 m	.489 m
$I_{c2}$	.49 m	.49 m
$V_{ec1}$	4.58 v	4.67 v
$V_{bc1}$	3.92 v	3.97 v
$V_{eb1}$	.66 v	.7 v
$V_{ce2}$	9.66 v	9.56 v
$V_{cb2}$	9.01 v	8.81 v
$V_{be2}$	.64 v	.7 v
$G_v$	154	200